

# Download Electricity Question Answers Chapter

Page No: 200. Q1. What does an electric circuit mean? Answer A continuous and closed path of an electric current is called an electric circuit. An electric circuit consists of electric devices, source of electricity and wires that are connected with the help of a switch. Electricity Chapter wise important question for Class 10 Science will help you in scoring more marks.. This consists of 1 mark Questions, 3 Mark Numericals Questions, 5 Marks Numerical Questions and previous year questions from Electricity Chapter. Answer: The given circuit is not complete. To complete the circuit, the positive terminal of the cell should be connected to one end of the switch, and the other terminal of the bulb should be connected to the other end of the switch. Download NCERT Solutions for Class 10 Science Chapter 12 Electricity PDF Question 3: Let the resistance of an electrical component remains constant while the potential difference across the two ends of the component decreases to half of its former value.